 



# Group 11 – Lab 1 report

Kim Svedberg (17%), Zebastian Thorsén (17%), Joen Järnkvist (17%),  
Sebastian Warzocha (17%), Christian Mokhtar (16%), Majd Sheikh Mahmoud (16%)


## Block Designs




Step 1

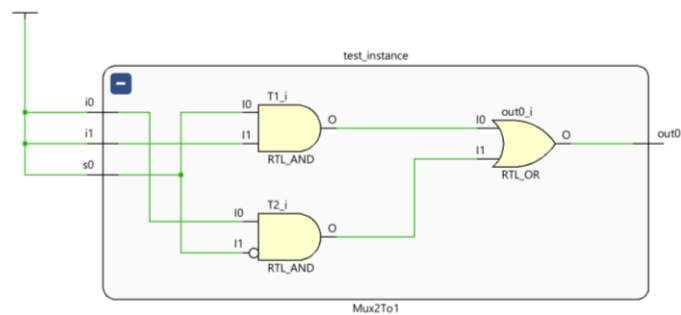


Step 2

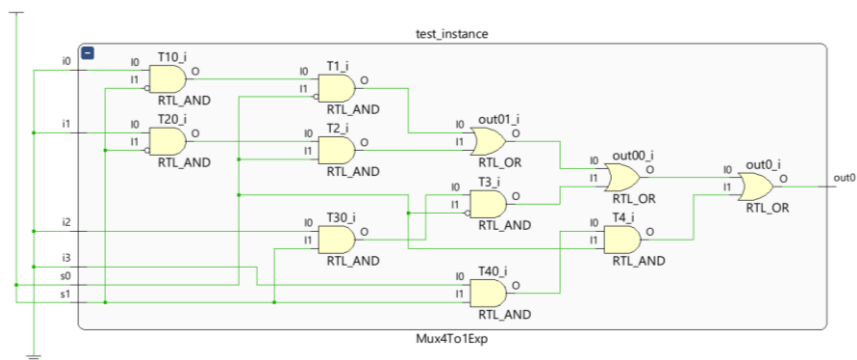

Step 3

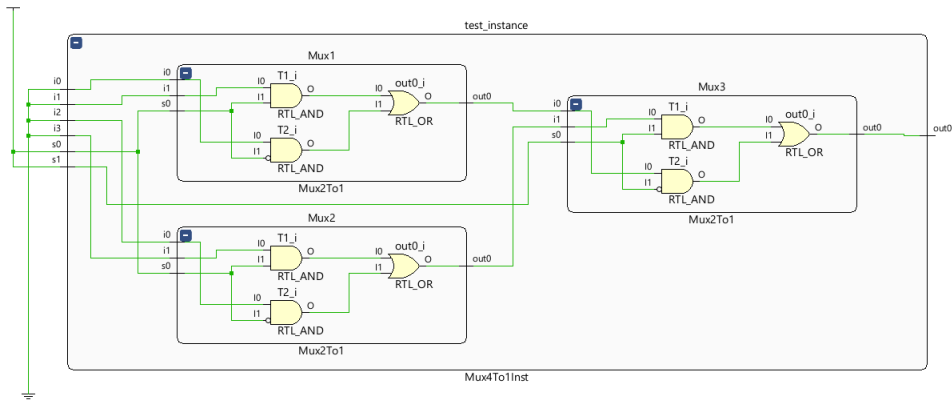


Step 4

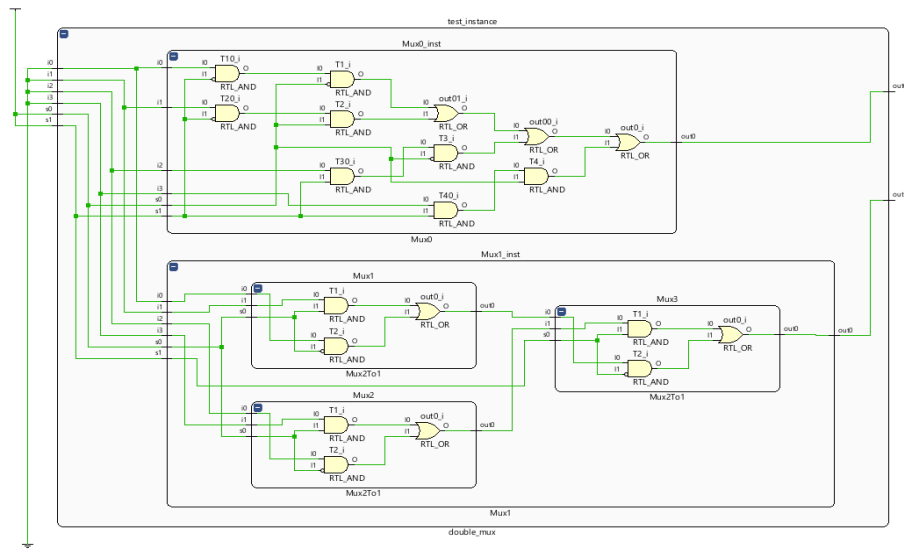


Step 5


## Simulations

 


Step 1

 


Step 2

 

Step 3

 

Step 4

 

Step 5

## LUT lists

Site Type	Used	Fixed	Prohibited	Available	Util%
Slice LUTs*	0	0	0	20800	0.00
LUT as Logic	0	0	0	20800	0.00
LUT as Memory	0	0	0	9600	0.00
Slice Registers	0	0	0	41600	0.00
Register as Flip Flop	0	0	0	41600	0.00
Register as Latch	0	0	0	41600	0.00
F7 Muxes	0	0	0	16300	0.00
F8 Muxes	0	0	0	8150	0.00

Step 1

Site Type	Used	Fixed	Prohibited	Available	Util%
Slice LUTs*	0	0	0	20800	0.00
LUT as Logic	0	0	0	20800	0.00
LUT as Memory	0	0	0	9600	0.00
Slice Registers	0	0	0	41600	0.00
Register as Flip Flop	0	0	0	41600	0.00
Register as Latch	0	0	0	41600	0.00
F7 Muxes	0	0	0	16300	0.00
F8 Muxes	0	0	0	8150	0.00

Step 2

Site Type	Used	Fixed	Prohibited	Available	Util%
Slice LUTs*	0	0	0	20800	0.00
LUT as Logic	0	0	0	20800	0.00
LUT as Memory	0	0	0	9600	0.00
Slice Registers	0	0	0	41600	0.00
Register as Flip Flop	0	0	0	41600	0.00
Register as Latch	0	0	0	41600	0.00
F7 Muxes	0	0	0	16300	0.00
F8 Muxes	0	0	0	8150	0.00

### Step 3

Site Type	Used	Fixed	Prohibited	Available	Util%
Slice LUTs*	0	0	0	20800	0.00
LUT as Logic	0	0	0	20800	0.00
LUT as Memory	0	0	0	9600	0.00
Slice Registers	0	0	0	41600	0.00
Register as Flip Flop	0	0	0	41600	0.00
Register as Latch	0	0	0	41600	0.00
F7 Muxes	0	0	0	16300	0.00
F8 Muxes	0	0	0	8150	0.00

### Step 4

Site Type	Used	Fixed	Prohibited	Available	Util%
Slice LUTs*	0	0	0	20800	0.00
LUT as Logic	0	0	0	20800	0.00
LUT as Memory	0	0	0	9600	0.00
Slice Registers	0	0	0	41600	0.00
Register as Flip Flop	0	0	0	41600	0.00
Register as Latch	0	0	0	41600	0.00
F7 Muxes	0	0	0	16300	0.00
F8 Muxes	0	0	0	8150	0.00

### Step 5